Section 427 Issue No. 2 November 1965

APPLICATION AND USE OF VOICE FREQUENCY REPEATERS FOR SUBSCRIBER LOOPS

CONTENTS

- 1. GENERAL
- 2. PRINCIPLE OF REPEATER OPERATION
- 3. REPEATER TRANSMISSION CHARACTERISTICS
 4. APPLICATION CONSIDERATIONS
- 5. EXPECTED REPEATERED CIRCUIT PERFORMANCE

TABLES I-III CHARTS I-II FIGURES 1-13

1. GENERAL

- 1.1 This section provides REA borrowers, consulting engineers, contractors, and other interested parties with technical information for use in the design and construction of REA borrowers' telephone systems. It discusses in particular the use of voice frequency repeaters in subscriber loop applications for use in laying out new plant or in the upgrading of existing facilities to meet the objectives of modern transmission.
- 1.2 The emphasis on the use of the economical fine gauge cables dictates increased use of electronic amplification to reduce losses. A very substantial amount of transmission loss is associated with these gauges. Voice frequency repeaters provide a low cost, high gain method for reducing losses. In conjunction with the high return loss available with D-66 loading, repeater gains of as much as 11 db are practical. Furthermore, because a repeater amplifies both the transmit and receive signals equally well, it not only raises the transmission level for the loop equipped with a repeater, but also helps improve the transmission of the overall connection. This is not true of one-way amplification devices which are also limited as to the useful amount of gain.
- 1.3 The design procedure used to engineer subscriber loop plant is treated in REA TE & CM-424, "Design of Two-Wire Subscriber Loop Plant," and reference should be made to that section. This section discusses (a) some of the more important characteristics of voice frequency repeaters (b) the application considerations for terminal repeaters located at the central office and intermediate repeaters at field mounted locations and (c) the transmission performance which is expected.
- 1.4 The type of repeater presently used for subscriber loop applications is the negative resistance type (abbreviated hereafter as NRR) but the design is not limited to this type repeater. Repeater use a different principle of operation and which provide equal performance and meet all subscriber application requirements can be used assuming their cost is comparable. The principle of operation NRR is discussed in paragraph 2.0 below.
- 1.5 For applications where the repeater will be located at the central office the NRR provides a of 7.0 db. Of this, approximately 0.4 to 0.5 db is lost in the LBO so that the total net ga the circuit is 6.5 db both in the transmit and receive directions. In terms of miles of loaded D-6 cable this represents 8.2 miles of 22 gauge cable and 5.4 miles of 24 gauge at 1000 cps. Therefore a C.O. mounted NRR is used, circuits can be extended in length by as much as the above values and transmission objectives are still met. The corresponding d-c loop resistance by which the outside is extended amounts to approximately 1500 ohms.
- 1.6 For applications where the repeater is used in a field mounted location the NRR provides a g of 11 db of which approximately 1.0 db is accounted for by the loss in two LBO's. This gair represents an extension in the outside plant of 11.2 miles of 22-D-66 or 8.3 miles of 24-D-66 load THRY THE PARTY OF cable, or 2000 ohms approximately in d-c loop resistance. 1 1 1 1 1 1 心传自己表示: 中国第一部产口的经生
- 1.7 The substantial amount of NRR gain used to engineer subscriber loops is a result of the unus impedance match possible with D-66 loading and the repeater impedance and this results in in and stable gain. This is not true of the H-88 loading system, particularly in the existing H-88 p had been engineered over the years on the basis of non-repeatered applications. Because substanti tions in cable mutual capacitance, load spacing accuracy and end-sections were built-in in existing plant by design, only a limited amount of gain is advisable if the circuits are to remain free of adverse effects of hollowness, echo, singing and frequency compression. LEAST STREET RESIDENCES

2. PRINCIPLE OF REPEATER OPERATION

- 2.1 The NRR is a two-wire repeater which amplifies transmit and receive voice frequency speech signals when used in a telephone line. It is inserted in series with the line in a manner so that tip and ring d-c line continuity is maintained and d-c (or a-c) supervisory signals and ringing currents pass through the repeater. Because the impedance of the bare cable is positive while that for the NRR is negative the net effect is that circuit loss is reduced. Thus the NRR amplifies signals by the principle of insertion of negative resistance in a line.
- 2.2 A transformer is used within the NRR to couple the repeater to the line and it is through this coupling (or line) transformer that d-c line continuity is maintained. There are two parts to that part of the repeater which furnishes the gain. These are the "series" repeater unit and the "shunt" repeater unit which make up the complete repeater known as the gain-unit. The series repeater unit is actually in series with the line fed from the line transformer while the shunt repeater unit is across the line coupled by capacitors or a shunt transformer in series with a capacitor. The gain unit of the NRR is shown in Figure 1.
- 2.3 Both the series and shunt repeater units furnish gain to the circuit but do so in a different manner. For example, it is possible to use the series part of the repeater alone to provide gain but this results in a poor impedance condition at the point in the circuit where the repeater is placed so that on toll calls the echo return loss performance is low resulting in talker echo (the talker hears his own voice delayed). To maintain high return loss values and provide the most gain possible both the series and shunt repeater units are used.
- 2.4 The NRR amplifies both the transmit and receive paths in a two-wire circuit by the same amount (unlike four-wire voice frequency repeaters or carrier systems which effectively have separate directions of transmission). Because of this ability the NRR type repeater is called "bilateral" and it presents the same impedance when viewed from either pair of terminals. Thus, its "in" and "out" terminals are interchangeable provided that the line building-out unit (LBO) described in paragraph 2.5 below always faces the cable in terminal repeater applications. Looking into the gain-unit of the NRR when the other pair of terminals is terminated in a 900 ohm resistor in series with a two microfarad capacitor, its impedance remains essentially the same; that is, 900 ohms in series with two microfarads. Therefore the NRR gain.
- 2.5 The line building-out unit (LBO) in the NRR is the remaining other important part of the repeater. It is a passive network consisting of coils, capacitors and resistors. Its sole purpose is to change the very complex impedance of the loaded cable pair which varies with frequency (and other factors) to a much simpler impedance such as a 900 ohm resistor, for example. When a cable pair is thus modified by the LBO to look like a simple 900 ohm resistor, very good performance results when the repeater gain unit is inserted in the cable because the repeater gain unit also looks like a 900 ohm resistor so that
- 2.6 The LBO in the NRR contains a capacitor building-out (BOC) component, a resistance building-out component (BOR), a high frequency corrector (HFC) and a low frequency corrector (LFC) as shown in Figure 2. All these contribute in smoothing out the complex impedance of the loaded cable and convert it to the simple resistance value discussed in paragraph 2.5 above. For the type of NRR normally used in this section for engineering subscriber loop plant no adjustments in the LBO are required. The LBO comes pre-adjusted by the manufacturer. A different LBO is used with each type of loading. The NRR used in this section will accommodate LBO's for D-66 or H-88 loading with exchange cable.

3. REPEATER TRANSMISSION CHARACTERISTICS

- 3.1 The type of NRR used in this section to engineer subscriber loop plant is a two-wire transistorized unit powered from 48 volts unfiltered central office batteries with a current drain of 35 milliwith no degradation in performance. The NRR can be adjusted to give as much as 13 db gain. However, the particular types described herein can be fixed gain types providing 7.0 db for terminal applications with the unit mounted in a central office location and 11.0 db for intermediate or field mounted applications. No gain strapping is required for the fixed-gain type. The gain is two-way; that is, 7.0 or 11.0 db gain the transmit direction and the same amount in the receive direction.
- 3.2 Direct-current for talking battery and dial pulsing, supervisory signals and frequency selective or superimposed d-c ringing currents are passed through the repeater without serious impairment and without the aid of auxiliary bypass equipment. Voice frequency tone signaling is improved when using NRR's because these signals are amplified the same as voice currents. NRR adds approximately 60 ohms to the overall subscriber loop resistance. This should be added to the other resistance when determining the signaling limits of the central office equipment.
- 3.3 The NRR will operate properly with maximum metallic direct current in the line of 40 ma. The gain of the repeater is not affected by d-c loop current variations and the same gain is obtained even when the d-c loop current is zero as, for example, when testing over the lines. For field mounted applications the surrounding temperature should not exceed -20°F. or 140°F.

- 3.4 The repeater provides the same gain regardless of the talkers speech level. It does not clip and distort very weak or very loud speech signals. Because its maximum undistorted single frequency power output is +16 dbm, the repeater unit can be routinely tested directly with normal 0 dbm test tone input power level without compression. The gain of the NRR is effective across the entire voice frequency band and beyond so that testing for gain can be performed at any frequency of interest using standard 600 or 900 ohm test equipment.
- 3.5 The NRR will work properly when calls are made from one repeatered loop to another repeatered loop, when calls are made through VNL+2 toll connecting or EAS trunks also equipped with NRR's, other type voice frequency repeaters in a back-to-back fashion, or carrier derived circuits.
- 3.6 Signaling is still possible through an NRR repeatered loop when the power to the repeater is cut off. This is because the d-c line continuity is still maintained through the line transformer in the NRR although there will be no amplification. When the power is off the circuit loss increases by approximately the amount of repeater gain. Thus, during an emergency communication can still be provided.
- 3.7 Based on past experience, the protection characteristics of NRR's in withstanding lightning surges are excellent. Also they have extremely low maintenance based on the experience of several thousand repeater units.

4. APPLICATION CONSIDERATIONS

- 4.01 Subscriber loops in buried plant 1700 and 2000 ohms and greater outside plant d-2 loop resistance, D-66 loaded, require NRR's (1500 ohms and greater for H-88 loading) in order to meet transmission objectives. When the loop has "long" end-sections a repeater is used starting at 1700 ohms. With "short" end-section loops the repeater is used starting at 2000 ohms. For aerial cables the above values of resistance must be reduced by 12 percent.
- 4.011 A "short end-section" D-66 loaded loop is defined as a loop having the maximum number of loading coils which can be placed in that length. The subscriber end-section in a short end-section loaded loop can be between 2000 to 4500 feet. If the subscriber end-section in a short end-section loaded loop is less than 2000 feet it should be built-out with a .030 microfarad building-out capacitor.
- 4.012 A "long end-section" D-66 loop is defined as a loaded loop with as little as 4500 feet end-section after the last loading point but not exceeding 12 kf including all unisolated bridged taps.
- 4.013 For existing H-88 loaded plant to be repeatered with NRR's the maximum subscriber end-section length after the last loading point, including all unisolated bridge taps, should not exceed 6000 feet. Structural return loss measurements for the existing portion are furthermore recommended to verify that the as-built plant is free of impedance irregularities. Observing this precaution with existing H-88 plant will help eliminate the substandard transmission performance shown in Figure 13 when the NRR's are installed. It is recommended that the structural return loss measurements be made at the ACD stage, so that if the measure plant performance is not found to be sufficiently adequate the 4.5 db NRR gain recommended in paragraph 4.02 should be reduced to between 2.5 to 3.0 db. The structural return loss measurements are described in REA TE & CM-445, "How to Make Structural Return Loss Measurements," and reference should be made to that Section

4.02 C.O. Mounted Repeaters

- 4.021 Use terminal NRR's with 7.0 db gain using the distance range in Table I for one uniform gauge D-66.
- 4.022 Use terminal NRR's with 7.0 db gain using the resistance range in Table III for mixed gauges D-66.
- 4.023 For existing H-88 plant a NRR with 4.5 db gain should be placed at the central office starting at 1500 ohms. This will provide adequate transmission up to 2400 ohms. For assuring adequate bandwidth and for avoiding hollowness or near singing conditions it is strongly recommended that end sections be kept at 6000 feet total or <u>less</u>.

4.03 Field Mounted Repeaters

- 4.031 Use intermediate NRR's with 11.0 db gain using the distance range in Table II for uniform gauges and the resistance range in Table III for mixed gauges D-66.
- 4.032 Intermediate repeaters with H-88 are not recommended because on repeatered loop-to-loop calls their use results in frequency compression which degrades the transmission. This is shown in Figure 11 for ideal H-88 outside plant. Gains higher than 4.5 db are not recommended because of possible hollowness and near singing effects. In actual practice performance can be worse due to deviations in cable mutual capacitance, spacing deviations and other factors. Figure 13 shows the performance with such plant. The response is highly irregular, conversation sounds hollow and the quality of transmission very poor. The circuit is on the borderline of instability.
- 4.04 For a NRR operating in a terminal central office location one LBO only is required of the same type as the loading system used. The LBO must face the cable side of the repeater as shown in Figure 2(b)

faces the central office equipment. A jumper wire is used to connect the tip an faces the central office equipment. A sumper wire is used to connect the tip are tip and ring of the central office equipment. This jumper wire is known as a The tip and ring of the central office always be facing the C.O. side of the NRR. It always be return loss performance with the NRR. It Become interchanged by error circuit echo return loss performance will be possible or sing in addition. Terminal NRR's are mounted at the central office still pair at the MDF and the LLA equipment and d-c powered from 48-volt nominal Figure 2(b). The dummy LDO musc start of the C.O. side of the NRR. I become interchanged by error circuit echo return loss performance will be poor

4 .

This is shown in Figure 2(c). The "dummy" LBO is not used for the loaded cable outside plant facing each side of the repeater that is shown in Figure 2(c). The "dummy" LBO is not used for the loaded cable outside plant facing each side of the repeater that no specific capacitance (CBO) or resistance (ROP) ass ments will be necessary to the NRR LBO in capacitance (CBO) or resistance (BOR).

and the line such as the middle third of first such as the middle third of repeater units can be powered and housed in repeaters can be powered by normal A-C to D-C converter arrangements and should be For those areas where temperatures lower than -20°F, will be encountered the second state of the se with a heater to maintain normal repeated equipment operating temperatures higher than 100°F, will be encountered the equipment cabinet should be be a factor to consider before deciding on this

The name and the cable politic power the repeaters from the 48-volt central office batteries. The power feed pair tip and A hooster feed notes similar the repeater to and at the repeater location should be connected together in order to see the remark office and at the repeater rocation should be connected together in order to hoster feed power supply in the central office with the normal 48-volt office batteries for elevating the voltage and extend-this booster feed power supply can be either 24- or 48-feet in series with the ring side of the 48-volt an units, for a feed of 300 shows the arrangement for a number of MRR units, for a feed of 300 shows the arrangement for a paragraph 3.1 above, approximately 15 series sling with the normal 48-volt office batteries for elevating the voltage and extendvalue are required at the repeater location to assure proper repeater operation.

1 for connecting the 48 or 24-volt booster supply central office batteries for the power feed. Most types of NRR presently evel the simplex arrange this method is less everything to demonstrate the simplex arrange. ment their tase grand isolated from the Dattery gooding terminal so that the simplex arrangethe desired from lightning, power system failures, earth potential effects, etc.

the power feed errangement of paragraph 4.07 above to power a number of repeater units that the voltage at the repeater location will rise when removing some of the repeaters from the line. If this voltage is higher than 60 volts at the repeater location it may some approximately 200 came: 20 percent, 2 watts) to prevent the voltage from rising.

and "out" terminess and also on the d-c power feed. Because protection experience on field section of the model of the mod The Constitution of Carrier Equipment," for the A-C side of the converter

For algorithm reasons a long line adapter must be used on all buried plant loops 1700 ohms (and plant d-c loop resistance and 1500 ohms (and greater) with aerial cable plant. and greater) with aerial caple plant.

The serial caple plant caple plant.

The serial caple plant caple plant.

The serial caple plant caple plant.

The serial caple plant.

The serial caple plant. (telephone set transmitter) a 24-volt booster power supply must be used (in the line with buried plant loops 1700 ohms and greater and the line with supply must be used (in the line with buried plant loops 1700 ohms and greater and the line with supply when the booster power with the line with the line with supply must be used (in the line with booster is adequate in to 3000 ohms). for aerial cable plant. A long line adapter is required when the booster power last this voltage in the line. The 24-volt booster is adequate up to 3000 ohms per loops beyond this a 48-volt booster must be used for resistance. For loops beyond this a 48-volt booster must be used for all of the 24-volt. The state of loop resistance. For loops beyond this a 48-volt booster must be used for the 24-volt booster can also be used starting at 1700 ohms in lieu of the 24-volt booster it aids both the signaling and the transmission. A The velt booster can also be used starting at 1700 ohms in lieu of the 24-volt booster it aids both the signaling and the transmission. A with the 48-volt booster for insenting the voltage in the line. it aids both the signaling and the transmission inserting the voltage in the line.

and the state of ringers on the

Subscriber loop which are of direct importance for local and DDD

- .2 Circuit Bandwidth
- 13 Evenness of Response
- 14 Sidetone Level
- 15 Stability
- 16 Noise
- 17 Crosstalk
- 18 Echo Return Loss
- 19 Singing Point

echo return loss and singing point performance are of primary importance on connections involving the network.

- 2 The net loss to the farthest subscriber which is allowable at 1000 cps is 10 db including all losses and repeater gain(s). The 10 db loss is the worst net loss for the longest loop. All other loops lower (better) than this value. Typical net losses are shown in Figures 3-10.
- 3 Where D-66 loading is used circuit bandwidth will be good even for loops with as much as 12 KF end-sections. For loops with "short" end-sections (one-party service) which are fully loaded the band-lith will be extremely good because the 1000 cps and 3400 cps response is practically identical. Modern type telephone sets transmit well up to 3400 cps so that they are used to advantage. The bandwidth of pical D-66 loaded loops with NRR's and various end-section lengths is shown in Figures 3-10.
- .31 Long D-66 loops with NRR's under the condition of one long loop calling another such long loop are shown in Figures 8-10. In Figures 8 and 9 the repeaters are back-to-back at the central office. Figure 8 the deviation in the 1000 to 3000 cps response (the difference in the values of insertion loss tween these two frequencies) is approximately 2 db. As the amount of gain becomes larger or the circuit ngth becomes longer, the deviation in response becomes larger also. In Figure 9 this deviation is proximately 4 db. With the intermediate repeater configurations at 11 db gain each, respectively, and th LBO's on each side of the repeater, the deviation becomes still larger. Reference to Figure 10 snows is to be 5 db between 1000 to 3000 cps. This performance for subscriber loop plant is very good.
- .32 The discussion in paragraph 5.31 above leads to this important consideration. With D-66 loading, because the cutoff is approximately 4600 cps, it is possible to use the very fine gauges to advange and with several intermediate E-6 repeaters and as many as six LBO's and still obtain circuits having good bandwidth. In other words, under the worst conditions (long repeater loop calling another long speater loop) frequency compression does not become a problem with D-66 loops because of the wide band railable. With other types of loading systems, particularly with the H-88, this will not be the case, severe frequency compression results. This is shown in Figure 12 where two intermediate NRR's are nown. Whereas the insertion loss at 1000 cycles is only 7.5 db at 3000 cps it is 24 db. This is with leal, 3000 feet end-sections (curve A), ideal load coil spacing and ideal cable mutual capacitance. In second of 7.5 and 12 kilofeet the 3000 cps loss is 31.3 and 39.5 db, respectively.
- 5.33 H-88 loading will more likely be encountered with existing outside plants. It will therefore be more realistic to also account for (a) the load spacing deviations which will be the rule rather han the exception (b) the higher mutual cable capacitance furnished under older cable specifications and c) the possibility for some moisture in the cable. Because of these factors which are realistic for xisting H-88 loaded plant the frequency response shown in Figure 12 will be further degraded. At best, he resulting circuit bandwidth will be 300 cps to around 2200-2400 cps, and this is not considered good odern-day transmission. Considering that most new types of trunk carrier equipment are being designed o provide circuit bandwidths up to 3400 cps, 2300 cps transmission would be offering the subscribers xtremely poor service.
- 5.4 Reference to Figures 2-10 on repeater insertion gain and frequency response indicates that the curve for the repeatered loss of the subscriber loop is rather smooth. That is, it shows no pronounced teaks and valleys. Because of this smoothness the circuits have a natural and therefore pleasing talking quality. This is also characteristic of D-66 loading although the circuits are being operated with fairly ligh amounts of gain. The presence of peaks and valleys in the frequency response as was the case with corner transmission practices produces undesirable hollowness and near singing conditions in repeatered loops in the talking condition and this is poor transmission. It is very undesirable and psychologically listurbing to the subscriber. This is shown in Figure 13.
- 5.5 Telephone set sidetone on the NRR design shown is low. The absence of high sidetone level contributes to natural and pleasing transmission. The use of the 96-volt talking battery does not increase sidetone levels appreciably.
- 5.6 Repeatered circuits with NRR's are to be unconditionally stable and this method is called the "stability design" method. This means that at no time during the progress of a call a subscriber experiences singing conditions or spurts of singing and in the idle condition no crosstalk or tones are being induced into other cable pairs. From a maintenance standpoint, with circuits using the "stability" design, little attention need be paid to the repeaters because they behave as passive elements, like cable, design, little strentien need be paid to the repeaters because they behave as passive elements, like cable, for example. Thus, maintenance personnel need not be particularly skilled in voice frequency repeater for examples. All the examples shown in Figures 3-10 are unconditionally stable.

- 5.7 Noise in subscriber loop plant is affected primarily by the type of construction used, the deg balance in the outside plant and the central office equipment and the influence characteristic power lines in the immediate area. Therefore noise is not directly the result of having repeaters in noise on its own. Such a balanced repeater merely amplifies whatever noise is already on the line by and reference should be made to that section for details. REA TE & CM-451, "Telephone Line Noise Mitigation and Measurement," discusses procedures for solving noise problems.
- 5.8 Crosstalk is controlled within limits by keeping the repeater gain at the central office locatic less than 8.0 db when the cables are D-66 loaded and by the crosstalk requirements for the cable the REA PE Specifications. For intermediate repeaters the crosstalk limit is increased because of the intervening cable loss between the central office and the repeater. Therefore from a crosstalk standpoint of pole mounted NRR's can be higher without problems.
- Figures 3-5 show typical values of ERL of as much as 28 db and 16 db for SP between 900 ohms in series with a 2 microfarad termination. ERL and SP requirements for two-wire VNL+2 toll connecting true are 18 db and 10 db, respectively. Therefore the performance of the loop plant with respect to these parameters is at least as good and actually better using this test termination. Performance using teles and SP 10 db. Performance characteristics using telephone set so these teles. At very low net loss (less than 2 db) the ERL is 16. For H-88 loops particularly with existing plant performance may not be adequate. Esho return loss values will be much lower, particularly the performance in the SP range at frequencies higher than 2500 cps.

TABLE I

RANGE OF DISTANCES FOR C.O. MOUNTED NRR'S
ONE UNIFORM GAUGE ONLY
EXCHANGE CABLE .083 MF/MI NOMINAL
BURIED PLANT ONLY

TH "SHORT" END-SECTION	NR	R DISTANCE	RANGE
ART PLACING REPEATER AT:	7.1 MI 12.4 MI	(37.5 KF) (65.6 KF)	24-D-66 24-D-66
ART PLACING REPEATER AT: MIT SAME REPEATER TO :	11.2 MI 19.6 MI	(59.2 KF) (103 KF)	22-D-66 22-D-66
TH "LONG" ² END-SECTION			
PART PLACING REPEATER AT:		\ J	24-D-66 24-D-66
PART PLACING REPEATER AT:			22-D-66 22-D-66
	MIT SAME REPEATER TO: ART PLACING REPEATER AT: MIT SAME REPEATER TO: TH "LONG" END-SECTION ART PLACING REPEATER AT: MIT SAME REPEATER TO: CART PLACING REPEATER AT:	ART PLACING REPEATER AT: 7.1 MI MIT SAME REPEATER TO: 12.4 MI ART PLACING REPEATER AT: 11.2 MI MIT SAME REPEATER TO: 19.6 MI TH "LONG" END-SECTION ART PLACING REPEATER AT: 6.1 MI MIT SAME REPEATER TO: 10.7 MI CART PLACING REPEATER AT: 9.5 MI CART PLACING REPEATER AT: 9.5 MI	ART PLACING REPEATER AT: 7.1 MI (37.5 KF) MIT SAME REPEATER TO: 12.4 MI (65.6 KF) ART PLACING REPEATER AT: 11.2 MI (59.2 KF) MIT SAME REPEATER TO: 19.6 MI (103 KF) TH "LONG" END-SECTION ART PLACING REPEATER AT: 6.1 MI (32.2 KF) MIT SAME REPEATER TO: 10.7 MI (56.5 KF) CART PLACING REPEATER AT: 9.5 MI (50.2 KF)

TABLE II RANGE OF DISTANCES FOR FIELD MOUNTED NRR'S ONE UNIFORM GAUGE ONLY BURIED PLANT ONLY (3)

Α.	D-66	WITH "	SHORT",2	END-SECTI	ON		NR	R DIST	ANCE I	RANGE	
		START	PLACING	REPEATER PEATER TO	AT:	12.4 I 15.3 I		(65.6 (80.7		24-D-66 24-D-66	
				REPEATER PEATER TO	AT:			(103 K (1 2 7 K		22-D-66 22-D-66	
в.	D-66	WITH '	'LONG'' ²	END-SECTIO	DИ						
				REPEATER PEATER TO		10.7	IM IM	(56.5 (71.5	KF) KF)	24-D-66 24-D-66	
				REPEATER TO		16.8	MI MI	(89.1 (112.8	KF)	22-D-66 22-D-66	·))

- NOTES 1. FOR AERIAL PLANT REDUCE DISTANCE BY 12 PERCENT
 - 2. AS DEFINED IN PARAGRAPHS 4.011 and 4.012
 - 3. FOUR RINGERS MAXIMUM ONLY
 - 4. OTHER REQUIREMENTS IN PARAGRAPH 4.09 ALSO APPLY

TABLE III RANGE OF RESISTANCE FOR C.O. AND FIELD MOUNTED NRR's MIXED GAUGE CABLES D-66 LOADED EXCHANGE CABLE .083 MF/MI NOMINAL BURIED PLANT ONLY (1)

Manual Contract of the Contrac	REPEATER LOCATION	D-66 LOOP END SECTION LENGTH(2)		117	RR RESI	STANCE R	1
The state of the s	C.O.	SHORT	START PLACING REPEATER TO		2000 3500	OHMS OHMS	
STATE OF THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE PERSON NAMED IN COLUMN TWO IS NOT THE OWNER, THE OWNE	C.O.	LONG	START PLACING REPEATER LIMIT SAME REPEATER TO	AT:	1700 3000	OHMS OHMS	
Participation of the Control of the	FIELD	SHORT	START PLACING REPEATER LIMIT SAME REPEATER TO	AT:	3500 ³ 4300	OHMS OHMS	
The state of the s	FIELD	LONG	START PLACING REPEATER TO	AT:	3000 ³ 3800	OHMS OHMS	
Ł							

HOTES

- 1. FOR AERIAL CABLE REDUCE RESISTANCE BY 12 PERCENT
 2. AS DEFINED IN PARAGRAPHS 4.011 and 4.012
 3. FOUR RINGERS MAXIMUM ONLY.

- 4. OTHER REQUIREMENTS IN PARAGRAPH 4.09 ALSO APPLY


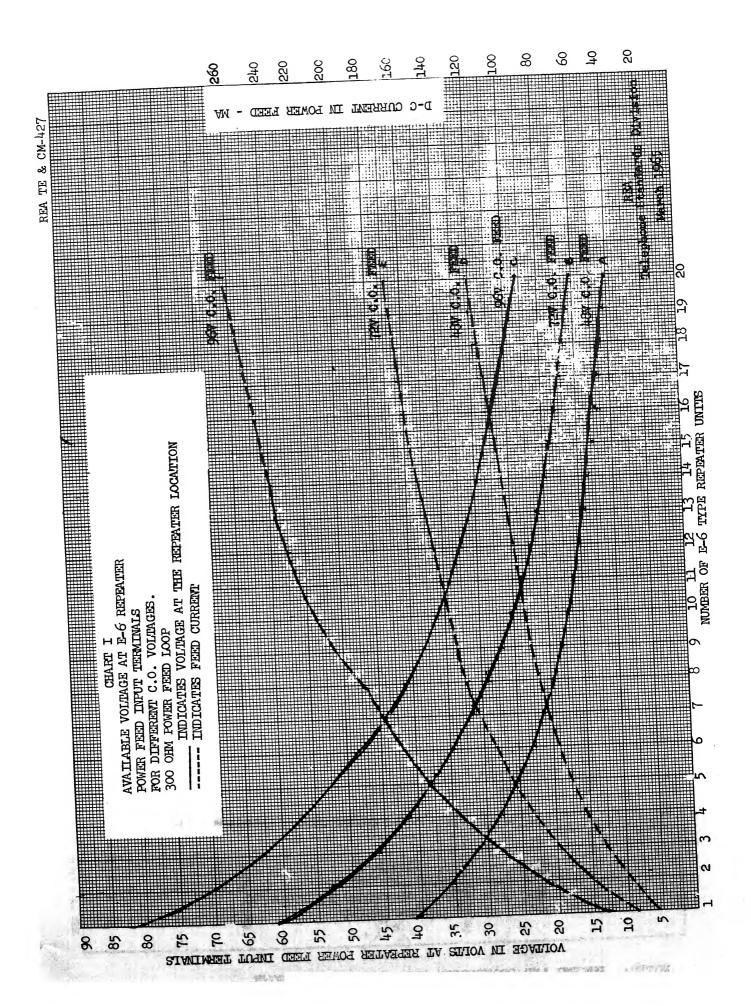



CHART II VARIOUS FOLER FEED ARRANGE ENTS FOR FOLE MOUNTED NRR'S USING SEPARATE CABLE PAIR FOR POWER FEED

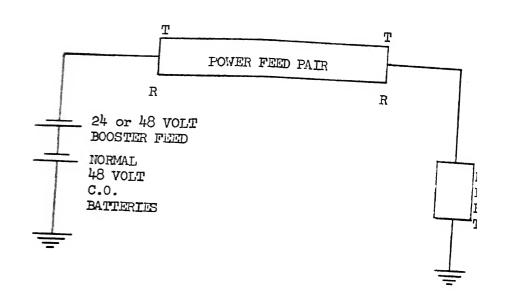



METHOD A


LONGITUDINAL FEED

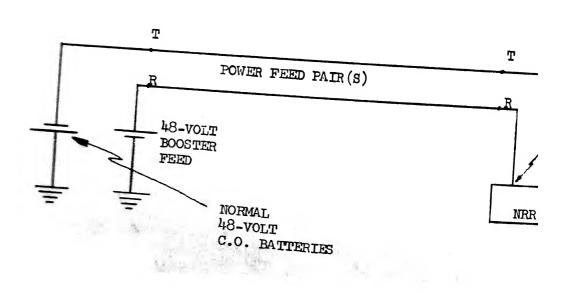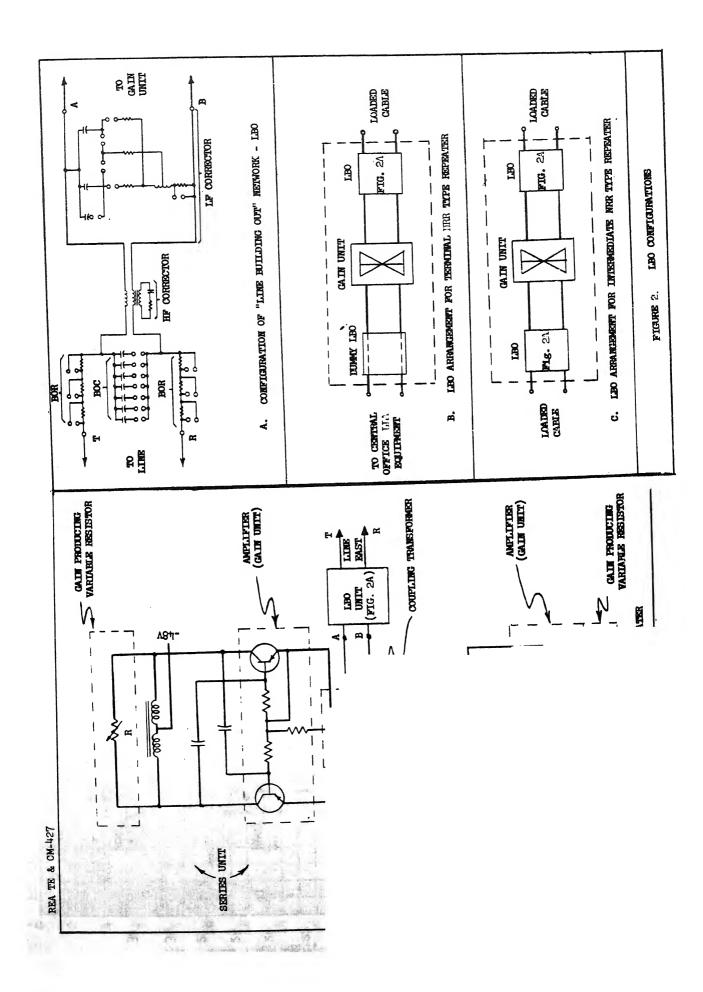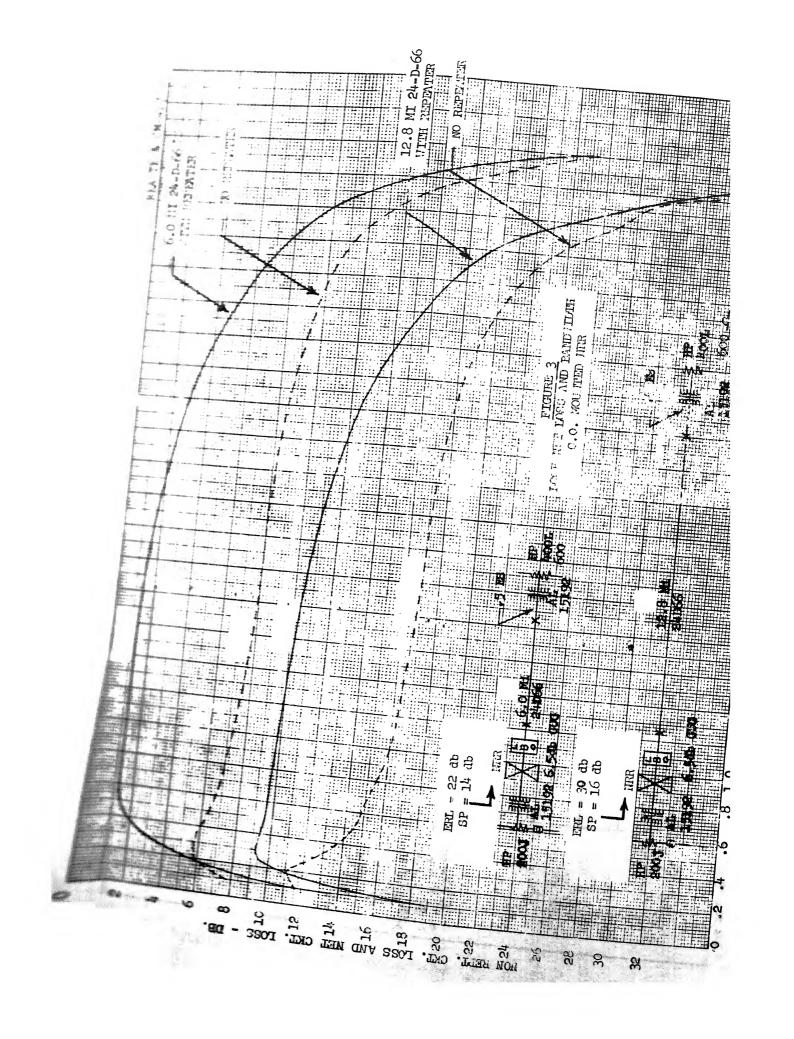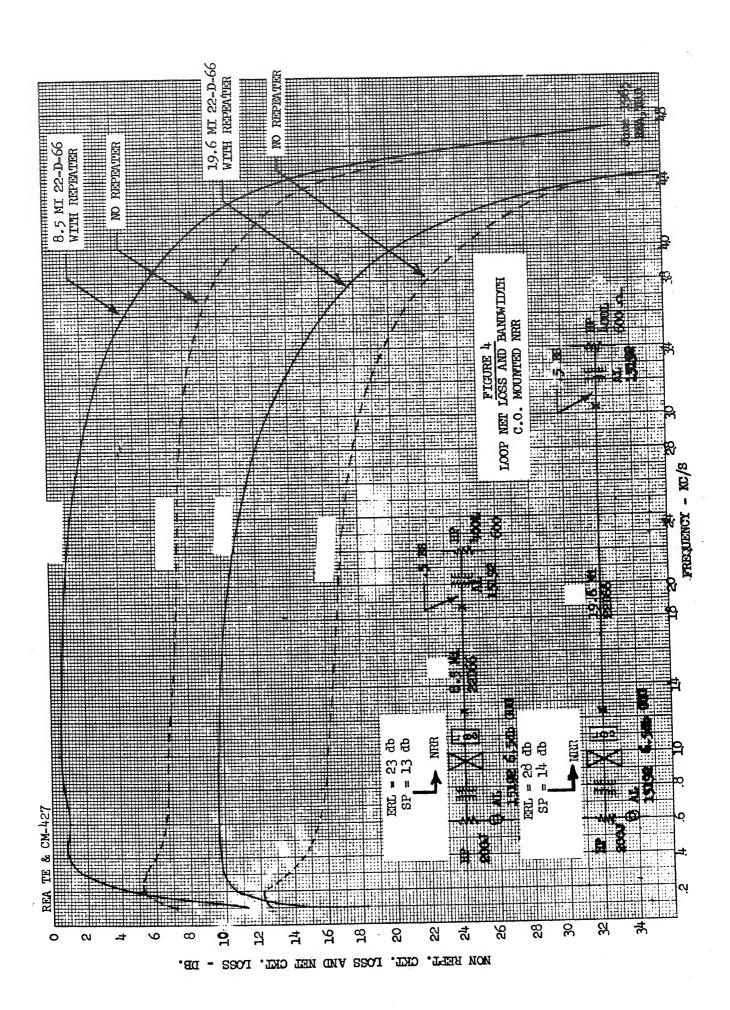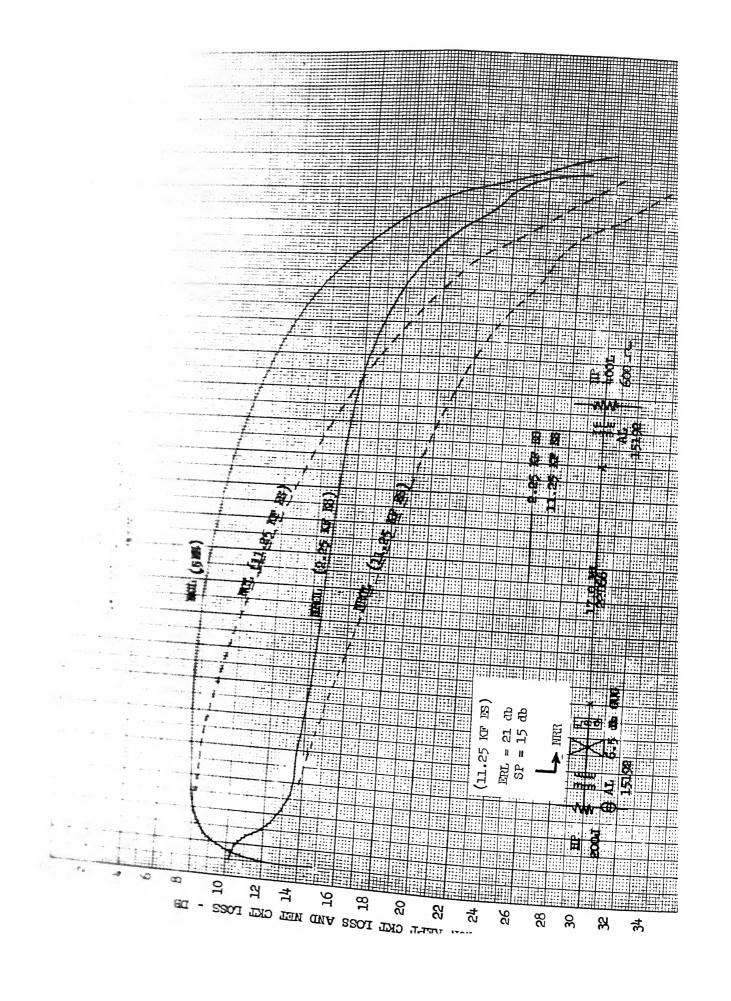
NRR CASE CAN BE GROUNDED TO GROUND TERMINAL

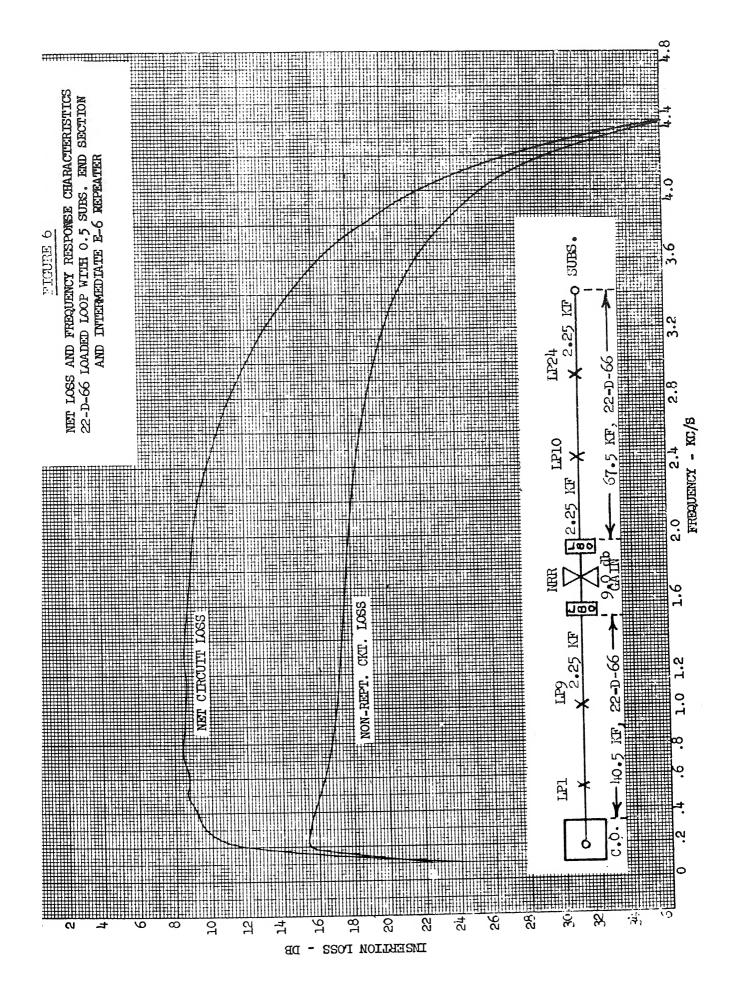


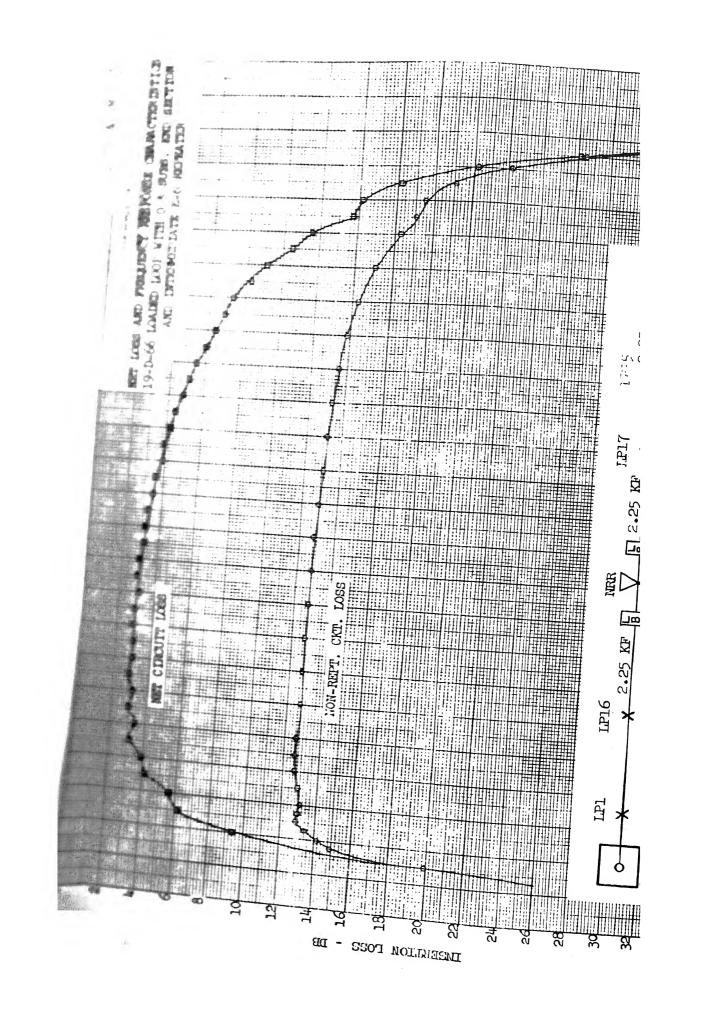


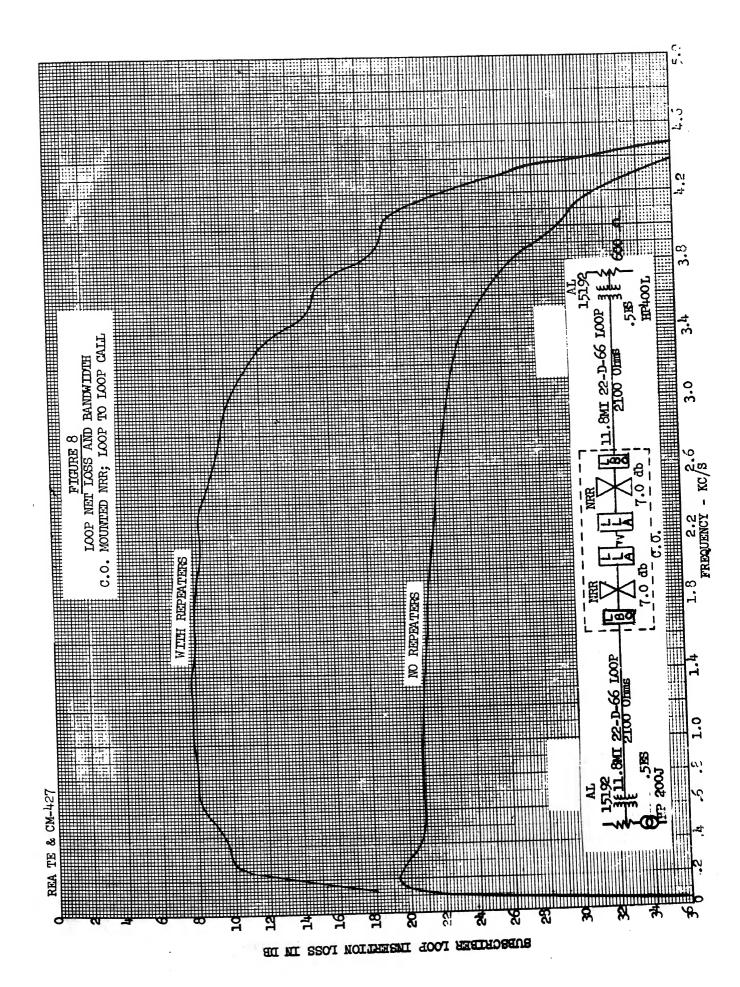


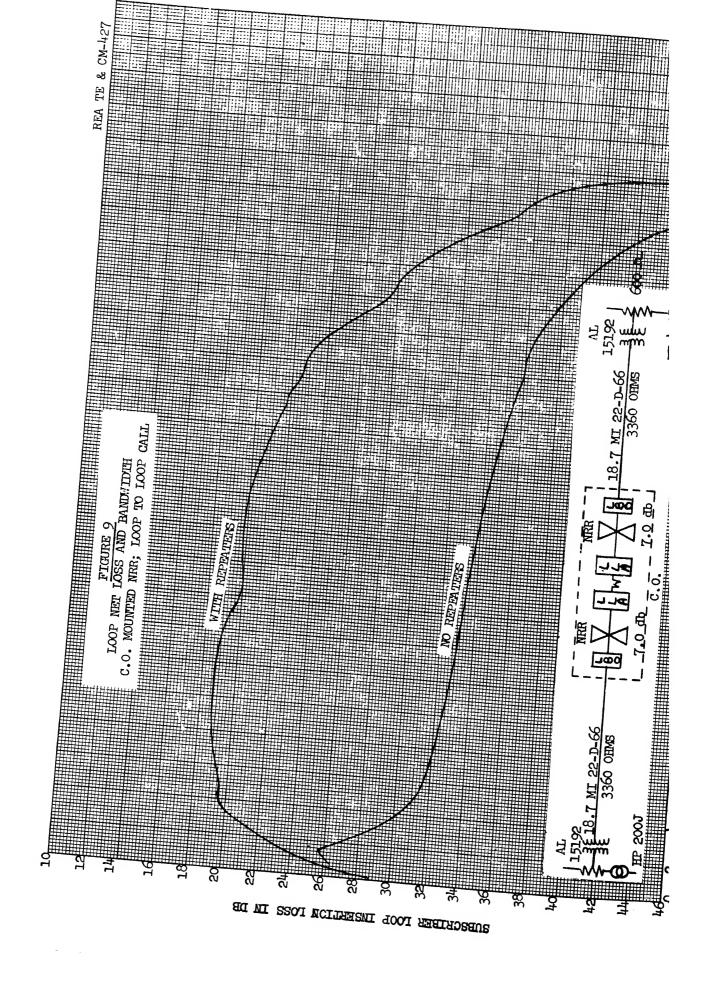













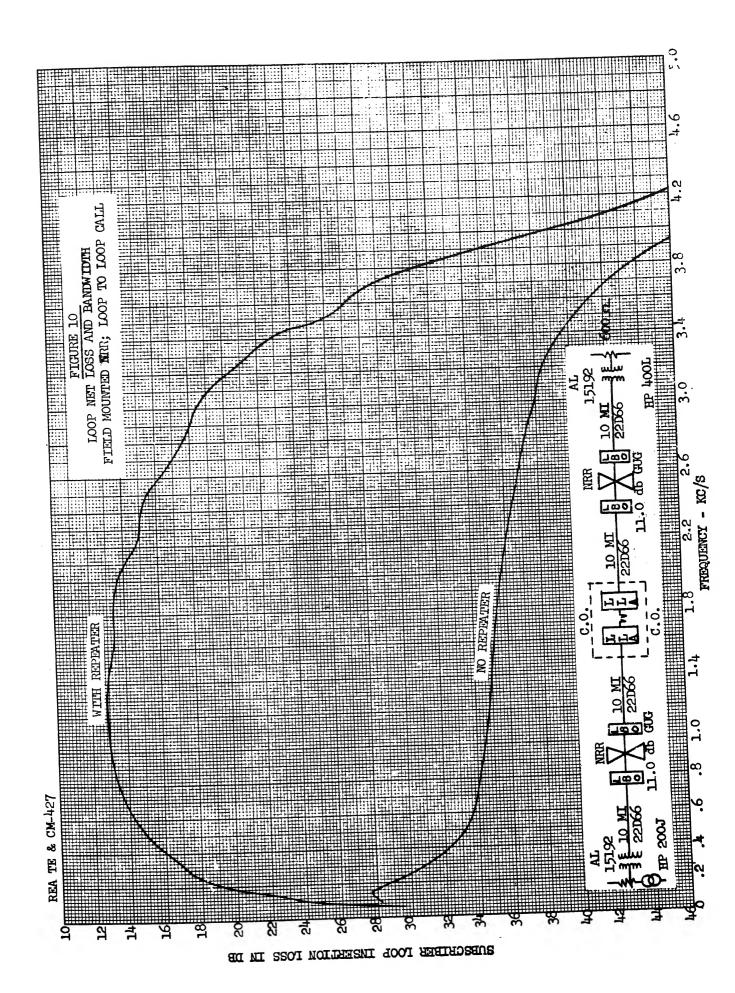


FIGURE 11
ECHO RETURN LOSS AND SINGING POINT PERFORMANCE
REPEATERED LOOP WITH TELEPHONE SET TERMINATION

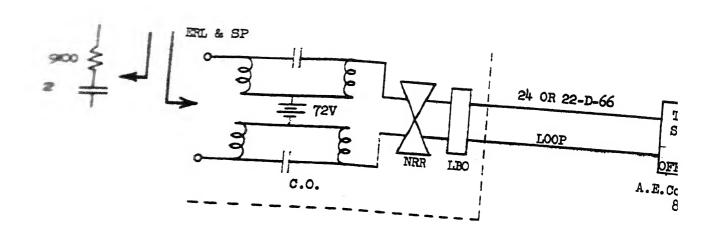

LOOP NET LOSS (db)	ECHO RETURN LOSS (db)	SINGING POINT
1.7	20.5	14
	10	
9.7		10
	18.5	
	16.5	12
	,	12
	<u>1088 (db)</u> 10	10 1.7 20.5 16 9.7

FIGURE 12

INSERTION LOSS - H-88 SUBSCRIBER LOOPS ONE INTERMEDIATE E-6 REPT PER LOOP

TWO LOOPS SWITCHED AT C.O. AND USING 96V BATTERY FEED DEAL MUTUAL CAPACITANCE (0.083 MF PER MILE) AND IDEAL SPACING (6000')

